 


**Figure 3.1 Op-amp equivalent circuit.** The two inputs are  $v_1$  and  $v_2$ . A differential voltage between them causes current flow through the differential resistance  $R_d$ . The differential voltage is multiplied by  $A$ , the gain of the op amp, to generate the output-voltage source. Any current flowing to the output terminal  $v_o$  must pass through the output resistance  $R_o$ .



**Figure 3.2 Op-amp circuit symbol.** A voltage at  $v_1$ , the inverting input, is greatly amplified and inverted to yield  $v_o$ . A voltage at  $v_2$ , the noninverting input, is greatly amplified to yield an in-phase output at  $v_o$ .



 


Figure 3.3 (a) An inverting amplified. Current flowing through the input resistor  $R_i$  also flows through the feedback resistor  $R_f$ . (b) A lever with arm lengths proportional to resistance values enables the viewer to visualize the input-output characteristics easily. (c) The input-output plot shows a slope of  $-R_f / R_i$  in the central portion, but the output saturates at about  $\pm 13$  V.

 


(a)

 


(b)


Figure E3.1 (a) This circuit sums the input voltage  $v_i$  plus one-half of the balancing voltage  $v_b$ . Thus the output voltage  $v_o$  can be set to zero even when  $v_i$  has a nonzero dc component. (b) The three waveforms show  $v_i$ , the input voltage;  $(v_i + v_b/2)$ , the balanced-out voltage; and  $v_o$ , the amplified output voltage. If  $v_i$  were directly amplified, the op amp would saturate.

 




**Figure 3.4** (a) A follower,  $v_o = v_i$ . (b) A noninverting amplifier,  $v_i$  appears across  $R_i$ , producing a current through  $R_i$  that also flows through  $R_f$ . (c) A lever with arm lengths proportional to resistance values makes possible an easy visualization of input-output characteristic. (d) The input-output plot shows a positive slope of  $(R_f + R_i)/R_i$  in the central portion, but the output saturates at about  $\pm 13$  V.

**Figure 3.5** (a) The right side shows a one-op-amp differential amplifier, but it has low input impedance. The left side shows how two additional op amps can provide high input impedance and gain. (b) For the one-op-amp differential amplifier, two levers with arm lengths proportional to resistance values make possible an easy visualization of input-output characteristics.

 

 

**Figure 3.6** (a) Comparator. When  $R_3 = 0$ ,  $v_o$  indicates whether  $(v_i + v_{\text{Ref}})$  is greater or less than 0 V. When  $R_3$  is larger, the comparator has hysteresis, as shown in (b), the input-output characteristic.

   


(a)

(b)


(c)

**Figure 3.7** (a) Full-wave precision rectifier. For  $v_i > 0$ , the noninverting amplifier at the top is active, making  $v_o > 0$ . For  $v_i < 0$ , the inverting amplifier at the bottom is active, making  $v_o > 0$ . Circuit gain may be adjusted with a single pot. (b) Input-output characteristics show saturation when  $v_o > +13$  V. (Reprinted with permission from Electronics Magazine, copyright © December 12, 1974; Penton Publishing, Inc.) (c) One-op-amp full-wave rectifier. For  $v_i < 0$ , the circuit behaves like the inverting amplifier rectifier with a gain of  $+0.5$ . For  $v_i > 0$ , the op amp disconnects and the passive resistor chain yields a gain of  $+0.5$ .



 


(a)

 


(b)


**Figure 3.8** (a) A logarithmic amplifier makes use of the fact that a transistor's  $V_{BE}$  is related to the logarithm of its collector current. With the switch thrown in the alternate position, the circuit gain is increased by 10. (b) Input-output characteristics show that the logarithmic relation is obtained for only one polarity;  $\times 1$  and  $\times 10$  gains are indicated.

   

 
**Figure 3.9 A three-mode integrator** With  $S_1$  open and  $S_2$  closed, the dc circuit behaves as an inverting amplifier. Thus  $v_o = v_{ic}$  and  $v_o$  can be set to any desired initial conduction. With  $S_1$  closed and  $S_2$  open, the circuit integrates. With both switches open, the circuit holds  $v_o$  constant, making possible a leisurely readout.

**Figure 3.10 Bode plot (gain versus frequency) for various filters.** Integrator (I); differentiator (D); low pass (LP), 1, 2, 3 section (pole); high pass (HP); bandpass (BP). Corner frequencies  $f_c$  for high-pass, low-pass, and bandpass filters.

 






**Figure E3.2** The charge amplifier transfers charge generated from a piezo-electric sensor to the op-amp feedback capacitor  $C$ .



**Figure 3.11 A differentiator** The dashed lines indicate that a small capacitor must usually be added across the feedback resistor to prevent oscillation.




**Figure 3.12 Active filters** (a) A low-pass filter attenuates high frequencies (b) A high-pass filter attenuates low frequencies and blocks dc. (c) A bandpass filter attenuates both low and high frequencies.

  


### Figure 3.13 Op-amp

#### frequency characteristics


early op amps (such as the 709) were uncompensated, had a gain greater than 1 when the phase shift was equal to  $-180^\circ$ , and therefore oscillated unless compensation was added externally. A popular op amp, the 411, is compensated internally, so for a gain greater than 1, the phase shift is limited to  $-90^\circ$ . When feedback resistors are added to build an amplifier circuit, the loop gain on this log-log plot is the difference between the op-amp gain and the amplifier-circuit gain.

 

  

 
**Figure 3.14 Noise sources in an op amp** The noise-voltage source  $v_n$  is in series with the input and cannot be reduced. The noise added by the noise-current sources  $i_n$  can be minimized by using small external resistances.

 




**Figure 3.15** The amplifier input impedance is much higher than the op-amp input impedance  $R_d$ . The amplifier output impedance is much smaller than the op-amp output impedance  $R_o$ .

**Figure 3.16 Functional operation of a phase-sensitive demodulator** (a) Switching function. (b) Switch. (c), (e), (g), (i) Several input voltages. (d), (f), (h), (j) Corresponding output voltages.





**Figure 3.17 A ring demodulator** This phase-sensitive detector produces a full-wave-rectified output  $v_o$  that is positive when the input voltage  $v_i$  is in phase with the carrier voltage  $v_c$  and negative when  $v_i$  is  $180^\circ$  out of phase with  $v_c$ .